

North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Name: digital logic design

Section: 3

Project Name: Design a pattern based digital lock system

Group Number: 3

Group members:		Score
Mohammad Olid Afzal	ID- 2011831042	
Ratul Dey	ID – 2014323642	
Mohamad Ashraful Islam Chowdhury	ID – 2014318642	
Ferdous Reza Niloy	ID- 2021281642	
Ratul Bhattacharjee	ID- 2012996642	

Project Contributions:

1. Mohamad Olid Afzal

ID- 2011831042

Work: 20% (4bit Magnitude Comparator, integration of pattern checker)

2. Ratul Dey

ID- 2014323642

Work: 15% (Decimal to BCD encoder and right shift register)

3. Mohamad Ashraful Islam Chowdhury

ID- 2014318642

Work: 15% (7 Segment Display)

4. Ferdous Reza Niloy

ID- 2021281642

Work: 30% (Main circuit, pattern checker, clock multiplier, Enabler, 4 bit memory block)

5. Ratul Bhattacharjee

ID- 2012996642

Work: 20% (Decimal to excess-1, BCD to excess-11 , 7 segment display)

Objectives:

Input: The users will be provided with a keypad for giving input to the system.


Output : There will be two types of 7 segments.

7 segment 1: Any input given through keypad will be displayed here.

7 segment 2: If the pattern is correct the result will be displayed in this 7 segment display. Result can be just a letter printed on the 7 segment (O/N).

Modes: A user will have two modes to operate the lock. In mode 1, the user can store a specific pattern. In mode 2, user can input a pattern that will be matched with stored pattern. Mode 1 is an advanced requirement and should be attempted only when mode 2 is complete. Mode 2 is the minimum requirement of the project.

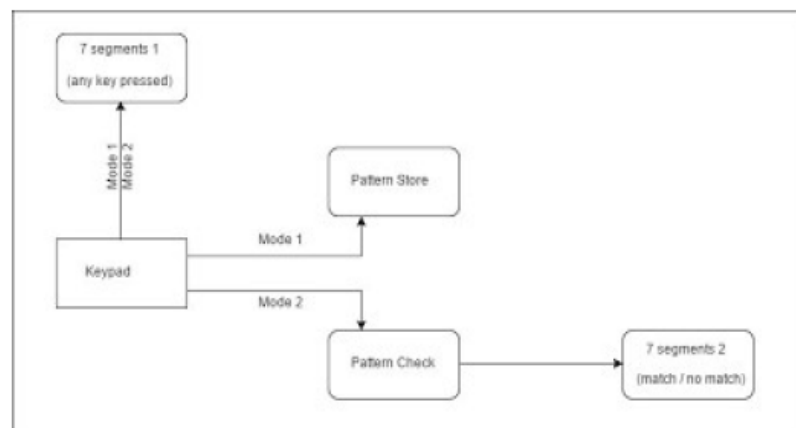Sample pattern: The pattern will be fixed for those completing only mode 1. It will consist of the 5 digits in following sequence - sec. no followed by group no and last 3 digits of ID. Say, If you are from Sec 5, Group 4 with an ID 13306996042 the fixed pattern will be 5 4 0 4 2. If different group members have different last 3 digits, you can pick one of them.



Block Diagram of the System

Circuits:

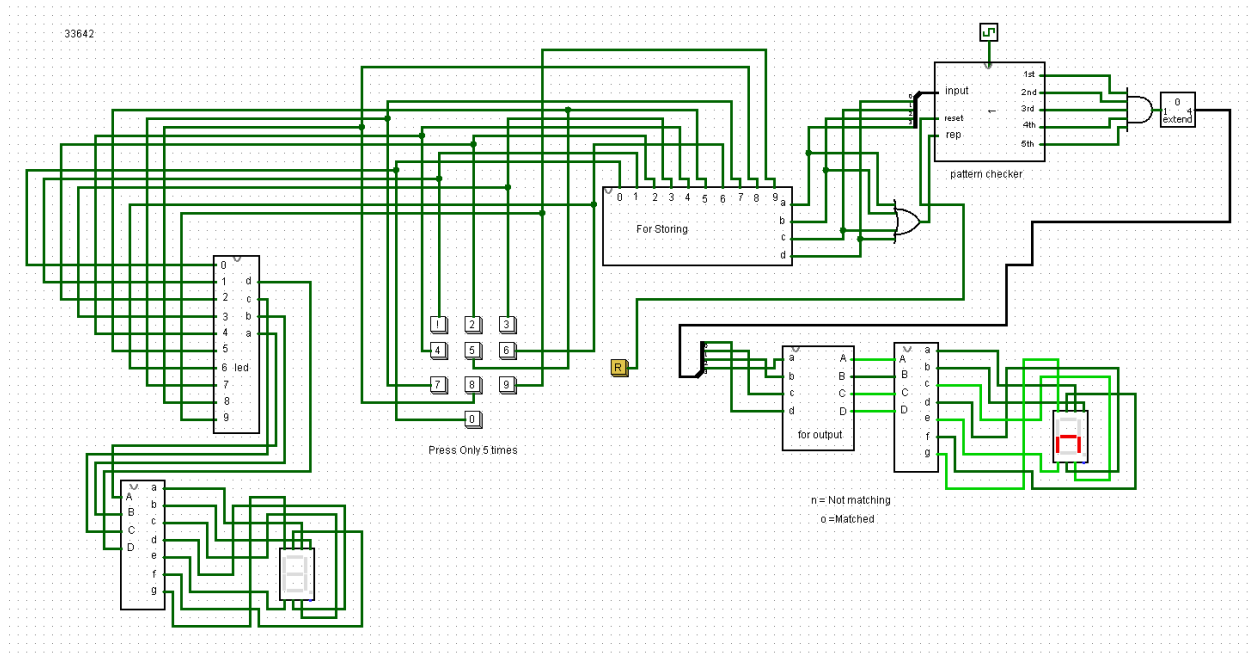


Figure: Main circuit

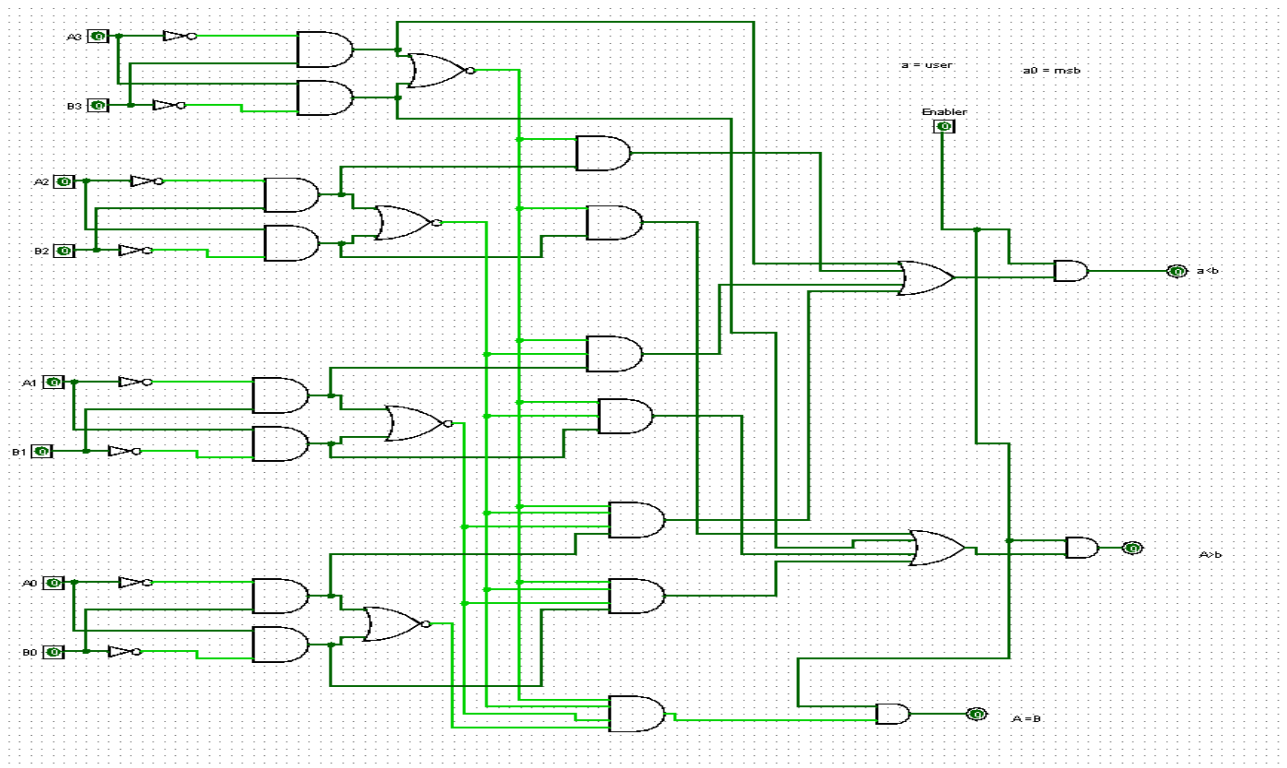


Figure: 4bit magnitude comparator

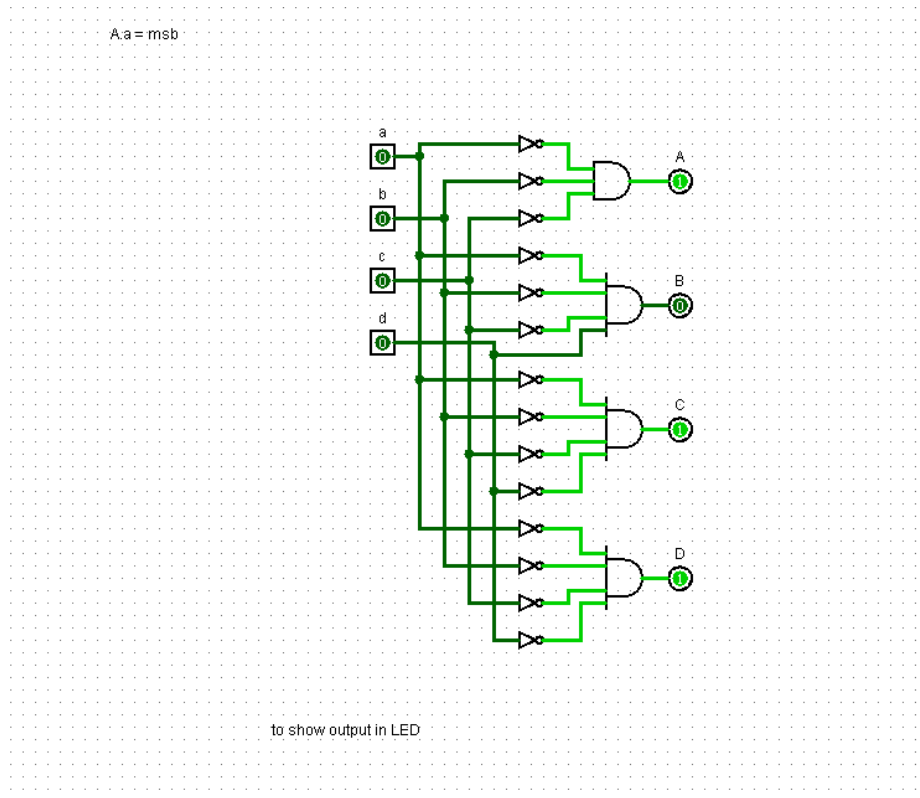
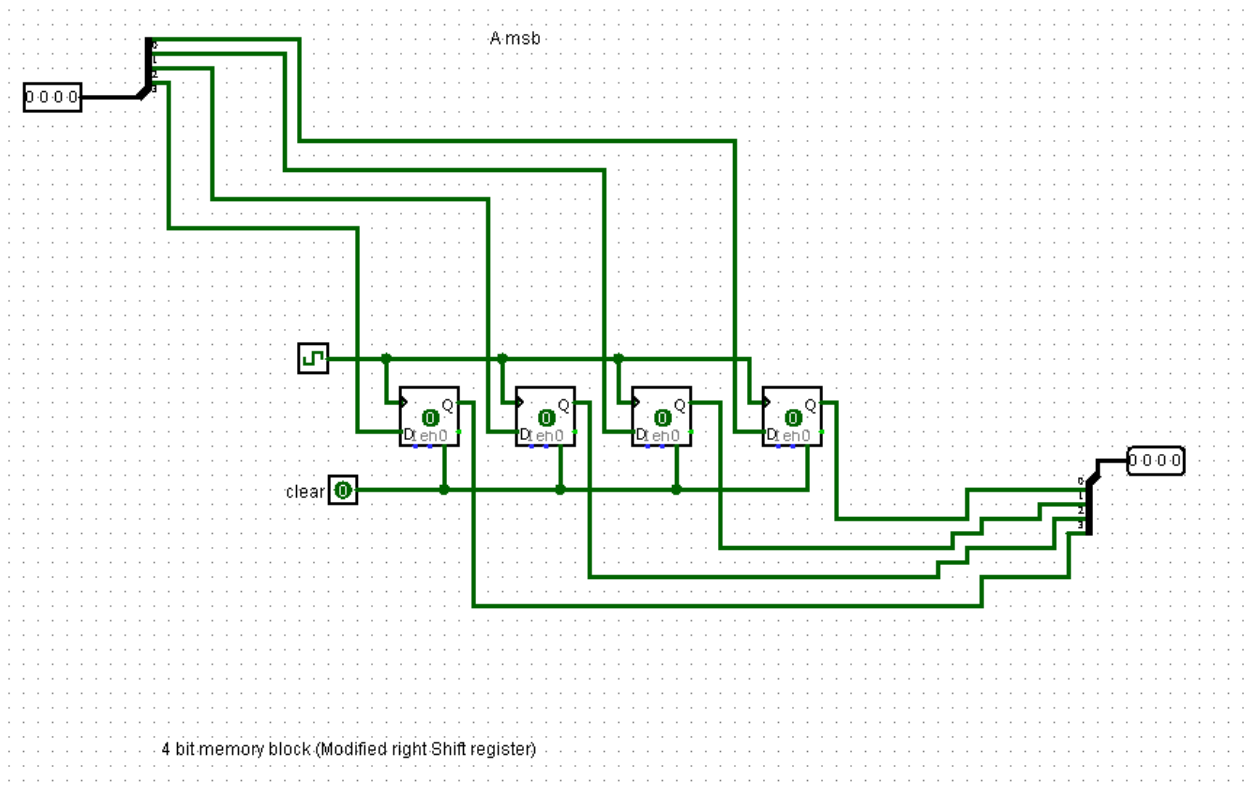


Figure: bcd to excess 11

 


Figure: Clock multiplier

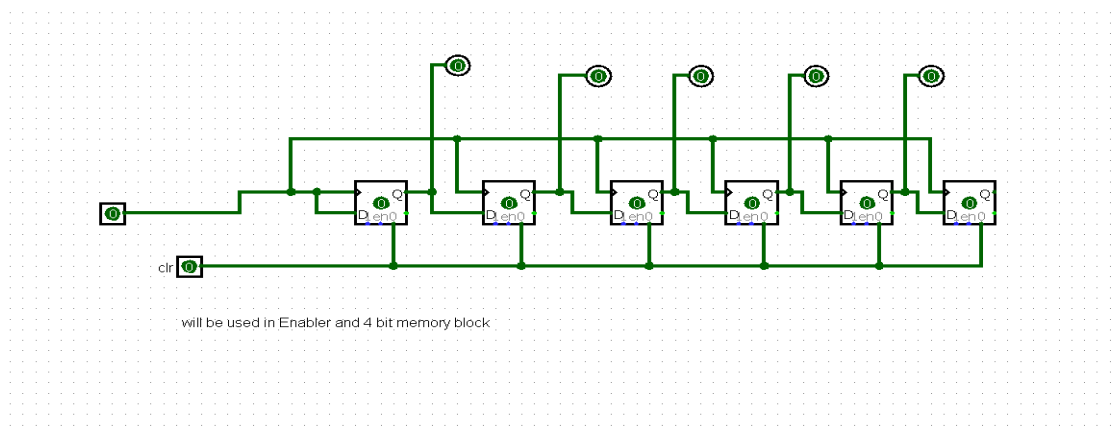


Figure: Right shift register

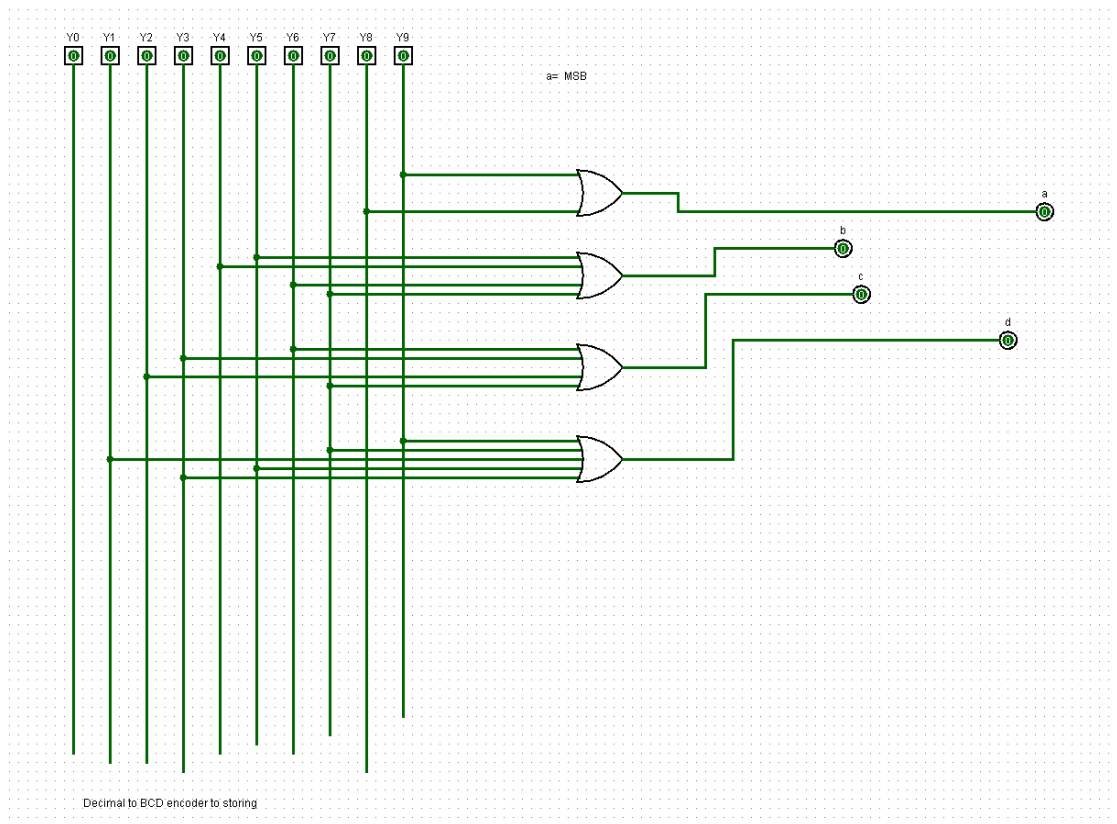


Figure: Decimal to bcd

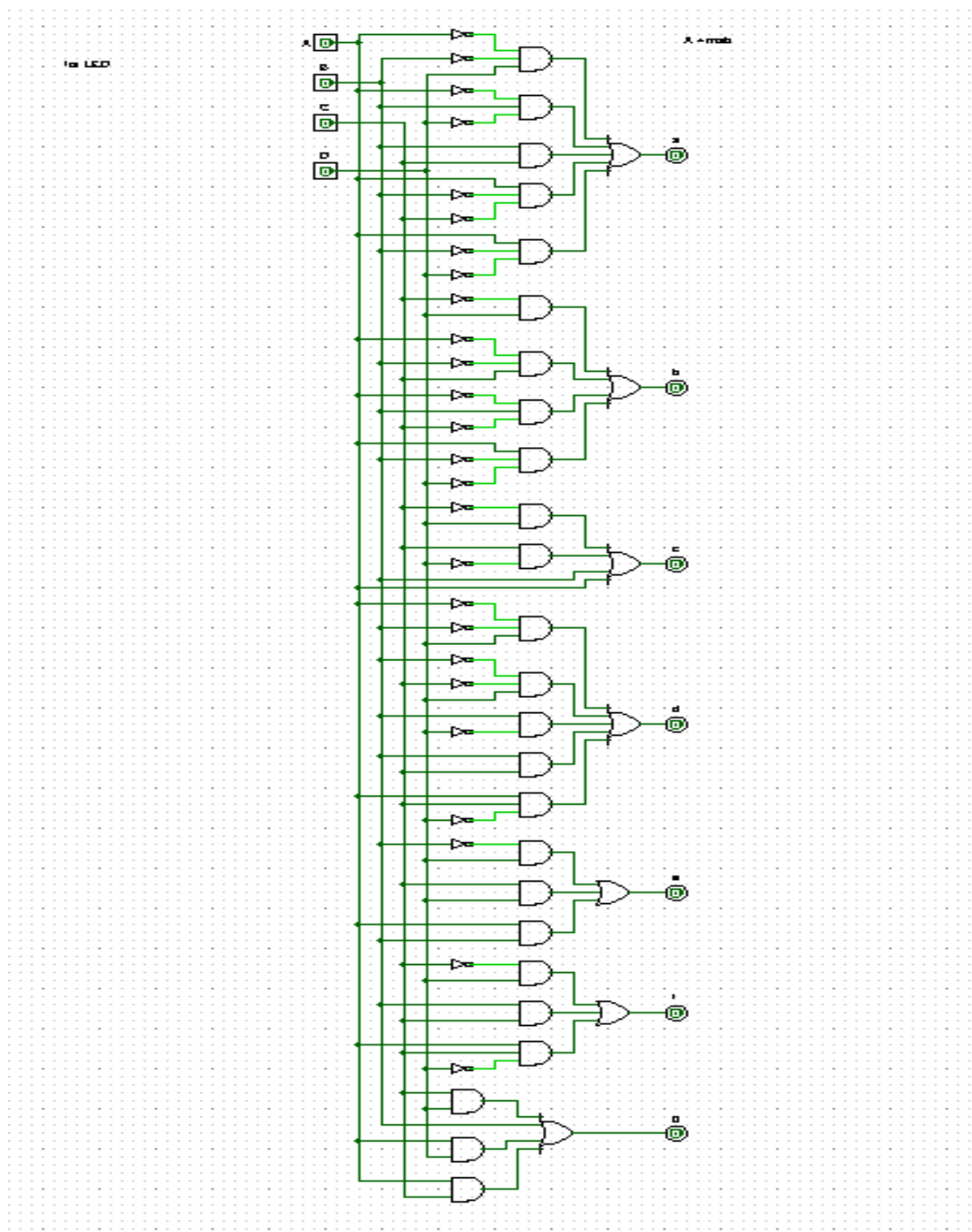


Figure: 7 segment display

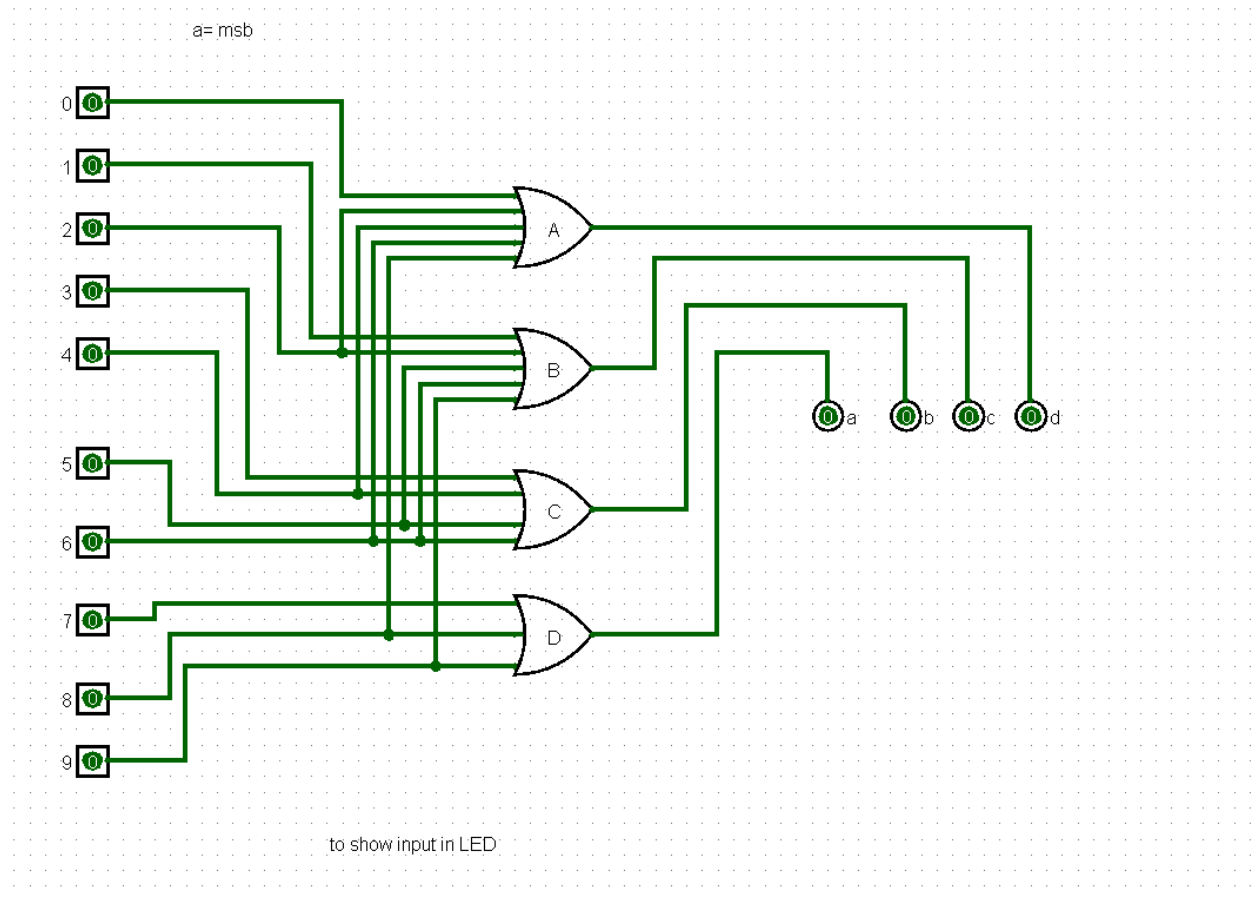


Figure: Decimal to excess 1

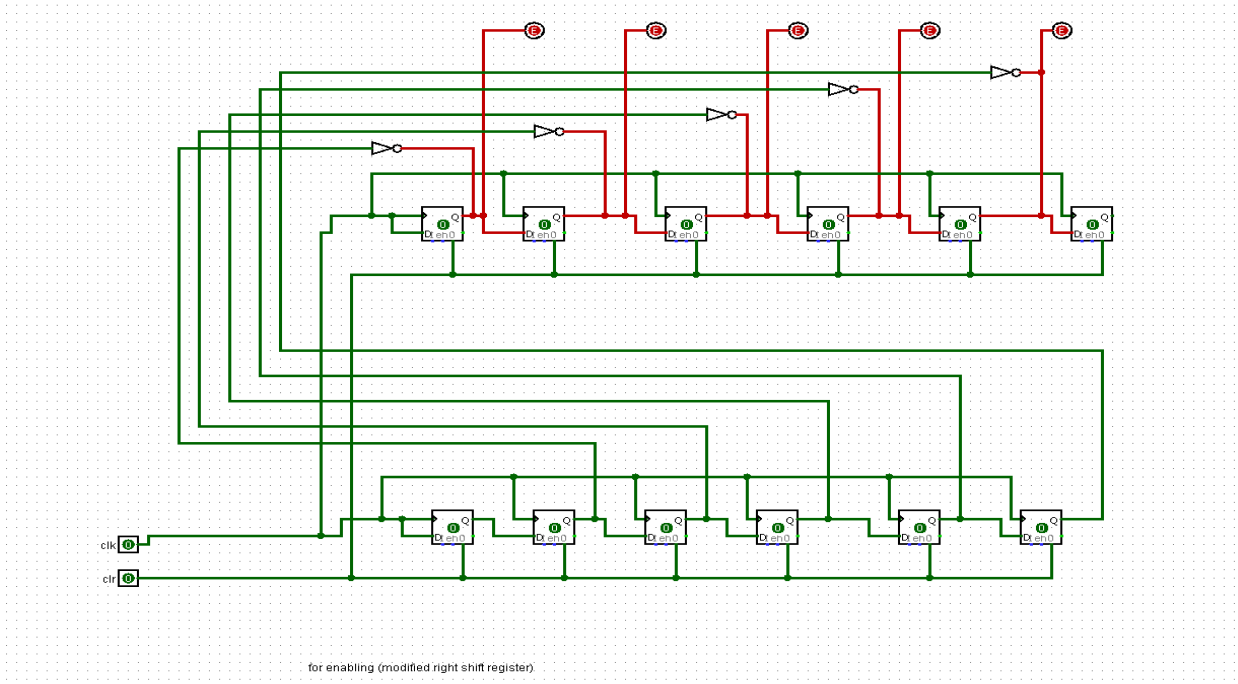


Figure: Enabler


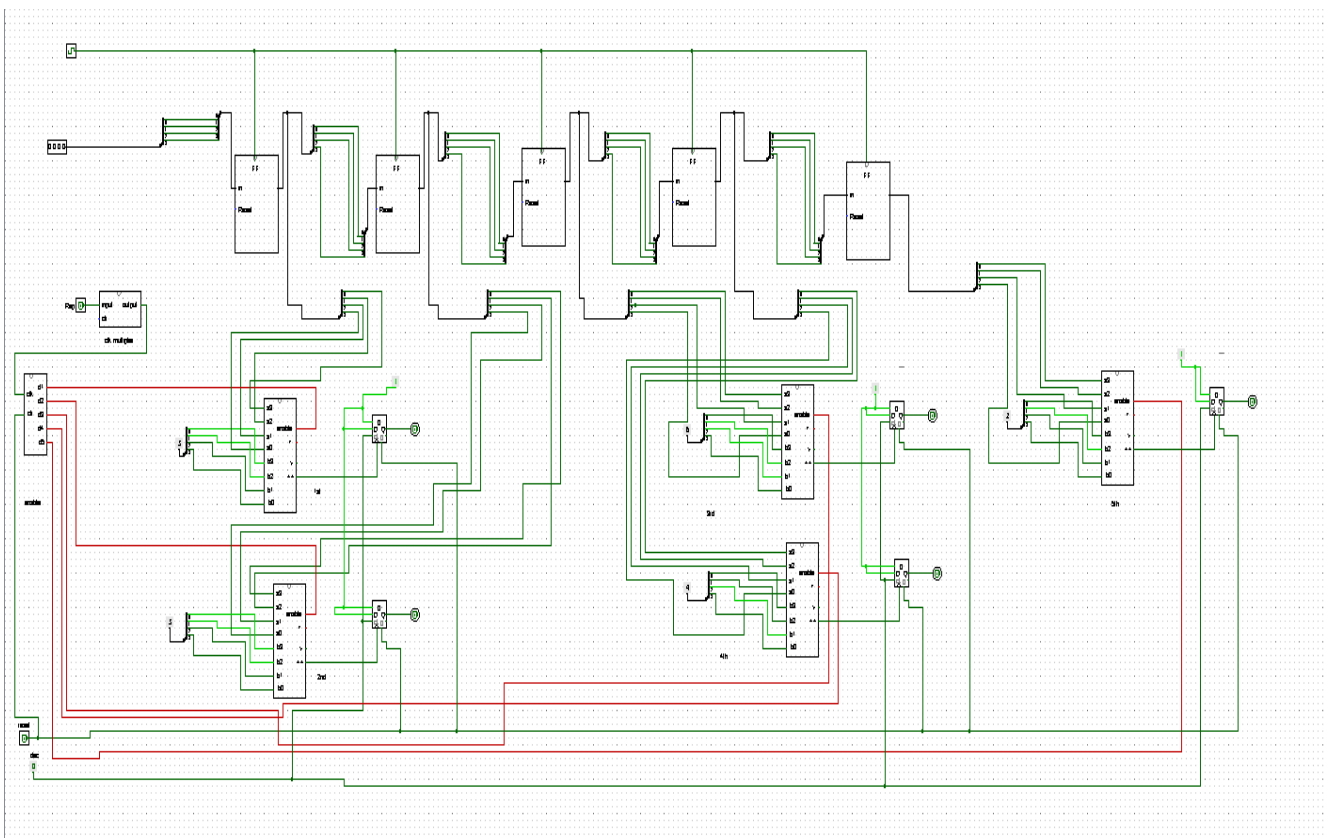


Figure: Pattern checker

Data tables:

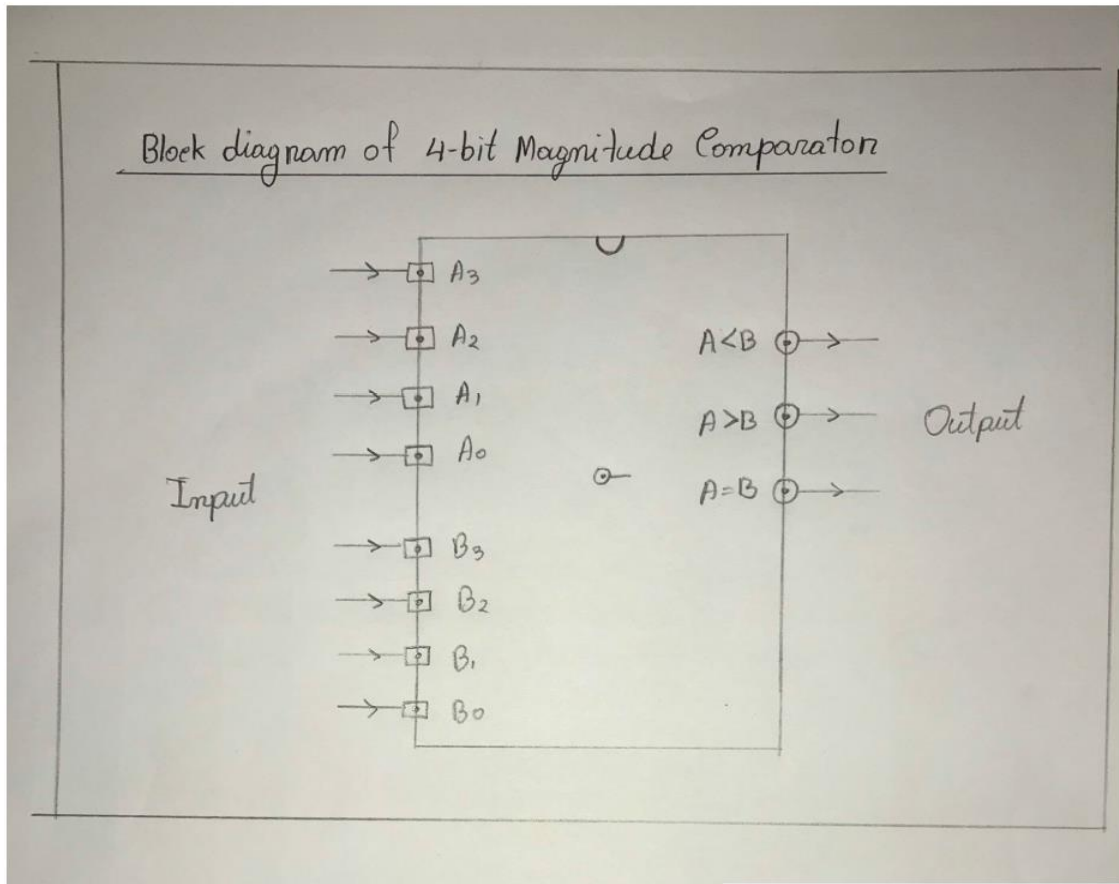

Truth Table of 4-bit Magnitude Comparator

[illegible]

Functions of 4-bit Magnitude Comparator

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$\text{if } A < B \rightarrow A_3 < B_3 \quad [A_3 = 0, B_3 = 1]$$

$$\rightarrow A_3 = B_3, A_2 < B_2$$

$$\rightarrow A_3 = B_3, A_2 = B_2, A_1 < B_1$$

$$\rightarrow A_3 = B_3, A_2 = B_2, A_1 = B_1, A_0 < B_0$$

$$\therefore A < B = \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0 B_0$$

$$\begin{bmatrix} X_3 = \bar{A}_3 B_3 \\ X_2 = \bar{A}_2 B_2 \\ X_1 = \bar{A}_1 B_1 \end{bmatrix}$$

$$\text{if } A > B \rightarrow A_3 > B_3 \quad [A_3 = 1, B_3 = 0]$$

$$\rightarrow A_3 = B_3, A_2 > B_2$$

$$\rightarrow A_3 = B_3, A_2 = B_2, A_1 > B_1$$

$$\rightarrow A_3 = B_3, A_2 = B_2, A_1 = B_1, A_0 > B_0$$

$$\therefore A > B = A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 \bar{B}_0$$


$$\begin{bmatrix} X_3 = A_3 \bar{B}_3 \\ X_2 = A_2 \bar{B}_2 \\ X_1 = A_1 \bar{B}_1 \end{bmatrix}$$

$$\text{and if } A = B \rightarrow A_3 = B_3, A_2 = B_2, A_1 = B_1, A_0 = B_0$$

$$\rightarrow X_3 + X_2 + X_1 + X_0$$

$$\begin{bmatrix} X_3 \Rightarrow A_3 = B_3 \\ X_2 \Rightarrow A_2 = B_2 \\ X_1 \Rightarrow A_1 = B_1 \\ X_0 \Rightarrow A_0 = B_0 \end{bmatrix}$$

Block Diagram of 7-segment

 

Seven Segment Decoder Truth Table

LED	INPUT				OUTPUT						
	A	B	C	D	a	b	c	d	e	f	g
NULL	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	1	0	0	1	1	0	0	0	0
2	0	0	1	1	1	1	0	1	1	0	1
3	0	1	0	0	1	1	1	1	0	0	1
4	0	1	0	1	0	1	1	0	0	1	1
5	0	1	1	0	1	0	1	1	0	1	1
6	0	1	1	1	1	0	1	1	1	1	1
7	1	0	0	0	1	1	1	0	0	0	0
8	1	0	0	1	1	1	1	1	1	1	1
9	1	0	1	0	1	1	1	1	0	1	1
a	1	0	1	1	0	0	1	0	1	0	1
0	1	1	0	0	0	0	1	1	1	0	1
12	1	1	0	1	x	x	x	x	x	x	x
13	1	1	1	0	x	x	x	x	x	x	x
14	1	1	1	1	x	x	x	x	x	x	x

Karnaugh Maps Simplification

AB\CD	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	0	X	X	X
10	1	1	0	1

$$a = A'B'D + A'BD' + AB'C' + ABD'$$

AB\CD	00	01	11	10
00	0	1	0	1
01	1	1	1	1
11	1	X	X	X
10	1	1	1	1

$$c = C'D + CD' + B + A$$

AB\CD	00	01	11	10
00	0	1	1	1
01	1	1	0	0
11	0	X	X	X
10	1	0	0	1

$$b = C'D + A'B'C + A'BC' + AB'D$$

AB\CD	00	01	11	10
00	0	1	1	0
01	1	0	1	1
11	1	X	X	X
10	0	1	0	1

$$d = A'B'D + B'C'D + BD' + BC + ACD'$$

AB\CD	00	01	11	10
00	0	1	1	0
01	0	0	1	0
11	1	X	X	X
10	0	1	1	0

$$E = B'D + CD + AB$$

AB\CD	00	01	11	10
00	0	1	0	0
01	0	1	1	1
11	0	X	X	X
10	0	1	0	1

$$F = C'D + BC + ACD'$$


AB\CD	00	01	11	10
00	0	0	1	0
01	1	1	1	1
11	1	X	X	X
10	0	1	1	1

$$G = CD + B + AD + AC$$

Truth table of Decimal to BCD encoder :-

Inputs										Outputs			
9	8	7	6	5	4	3	2	1	0	a	b	c	d
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

Block diagram of Decimal to BCD encoder

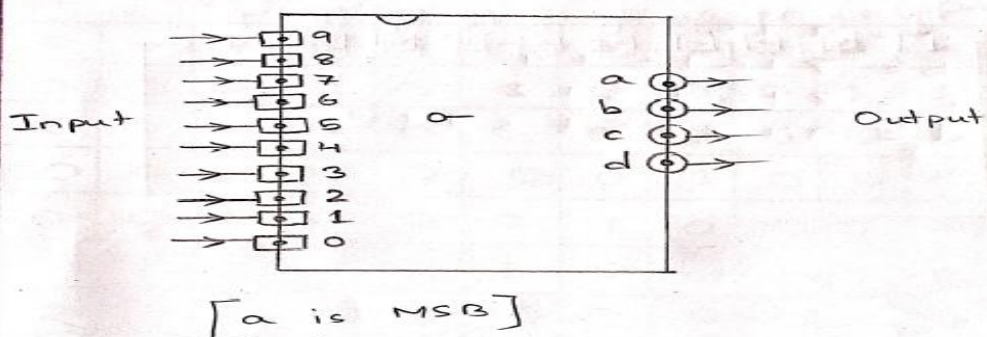

with table of Decimal to BCD conversion

Expression of a, b, c, d :-

$$a = 9 + 8$$

$$b = 7 + 6 + 5 + 4$$

$$c = 7 + 6 + 3 + 2$$

$$d = 9 + 7 + 5 + 3 + 1$$

Truth table of Decimal to BCD - excess-1.

Decimal	BCD	BCD Excess - 1			
		B ₃	B ₂	B ₁	B ₀
0	0000	0	0	0	1
1	0001	0	0	1	0
2	0010	0	0	1	1
3	0011	0	1	0	0
4	0100	0	1	0	1
5	0101	0	1	1	0
6	0110	0	1	1	1
7	0111	1	0	0	0
8	1000	1	0	0	1
9	1001	1	0	1	0

Expression for Circuit :

$$B_0 = 0 + 2 + 4 + 6 + 8$$


$$B_1 = 1 + 2 + 5 + 6 + 9$$

$$B_2 = 3 + 4 + 5 + 6$$

$$B_3 = 7 + 8 + 9$$

Block diagram of Decimal to BCD


Excess - 1 :

 

[Here, d is the MSB]

Block Diagram:

A msb , a msb

 

Block Diagram of BCD to BCD excess 11


BCD to BCD Excess-11

Decimal	BCD	BCD Excess-11			
		B3	B2	B1	B0
0	0 0 0 0	1	0	1	1
1	0 0 0 1	1	1	0	0

Right shifter using D flip-flops :

States	Input	Output
Initial state	X	XXXXXX
T1	1	1XXXXX
T2	0	01XXXX
T3	1	101XXX
T4	0	0101XX
T5	1	10101X
T6	0	010101

Block diagram for Right Shift register

 

right shift register